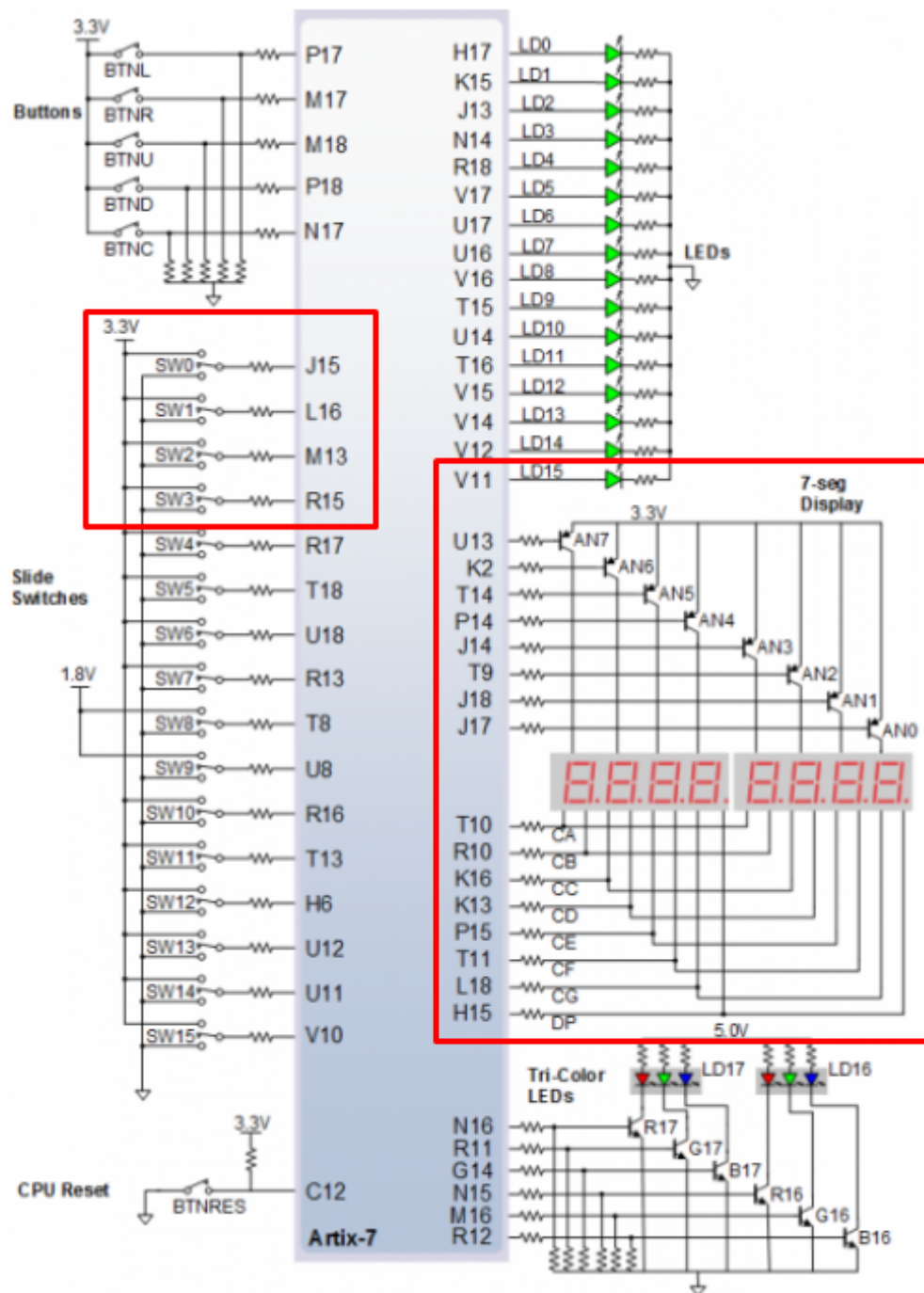


# Lab assignment 04 - Segment

## Prep. task - Decoder truth table for common anode 7-segment display

Hex	Inputs	A	B	C	D	E	F	G
0	0000	0	0	0	0	0	0	1
1	0001	1	0	0	1	1	1	1
2	0010	0	0	1	0	0	1	0
3	0011	0	0	0	0	1	1	0
4	0100	1	0	0	1	1	0	0
5	0101	0	1	0	0	1	0	0
6	0110	0	1	0	0	0	0	0
7	0111	0	0	1	1	1	1	1
8	1000	0	0	0	0	0	0	0
9	1001	0	0	0	0	1	0	0
A	1010	0	0	0	1	0	0	0
b	1011	1	1	0	0	0	0	0
C	1100	0	1	1	0	0	0	1
d	1101	1	0	0	0	0	1	0
E	1110	0	1	1	0	0	0	0
F	1111	0	1	1	1	0	0	0

## Prep. task - Schematic with connection of 7-segment displays on Nexys A7 board



## Listing of VHDL architecture from source file hex\_7seg.vhd with syntax highlighting

```

architecture Behavioral of hex_7seg is

begin
    p_7seg_decoder : process(hex_i)
    begin
        case hex_i is
            when "0000" =>

```

```

        seg_o <= "0000001";      -- 0
    when "0001" =>
        seg_o <= "1001111";      -- 1
    when "0010" =>
        seg_o <= "0010010";      -- 2

    when "0011" =>
        seg_o <= "0000110";      -- 3
    when "0100" =>
        seg_o <= "1001100";      -- 4
    when "0101" =>
        seg_o <= "0100100";      -- 5
    when "0110" =>
        seg_o <= "0100000";      -- 6
    when "0111" =>
        seg_o <= "0011111";      -- 7
    when "1000" =>
        seg_o <= "0000000";      -- 8
    when "1001" =>
        seg_o <= "0000100";      -- 9
    when "1010" =>
        seg_o <= "0001000";      -- A
    when "1011" =>
        seg_o <= "1100000";      -- b
    when "1100" =>
        seg_o <= "0110001";      -- C
    when "1101" =>
        seg_o <= "1000010";      -- d

    when "1110" =>
        seg_o <= "0110000";      -- E
    when others =>
        seg_o <= "0111000";      -- F
    end case;
end process p_7seg_decoder;

end Behavioral;

```

## Listing of VHDL stimulus process from testbench file tb\_hex\_7seg.vhd with syntax highlighting and asserts

```

p_7seg_decoder : process
begin
    s_hex <= "0000";
    wait for 100 ns;
    assert (s_seg = "0000001")
    report "Simulation unsuccessful for input: 0" severity error;

```

```
s_hex <= "0001";
wait for 100 ns;
assert (s_seg = "1001111")
report "Simulation unsuccessful for input: 1" severity error;

s_hex <= "0010";
wait for 100 ns;
assert (s_seg = "0010010")
report "Simulation unsuccessful for input: 2" severity error;

s_hex <= "0011";
wait for 100 ns;
assert (s_seg = "0000110")
report "Simulation unsuccessful for input: 3" severity error;

s_hex <= "0100";
wait for 100 ns;
assert (s_seg = "1001100")
report "Simulation unsuccessful for input: 4" severity error;

s_hex <= "0101";
wait for 100 ns;
assert (s_seg = "0100100")
report "Simulation unsuccessful for input: 5" severity error;

s_hex <= "0110";
wait for 100 ns;
assert (s_seg = "0100000")
report "Simulation unsuccessful for input: 6" severity error;

s_hex <= "0111";
wait for 100 ns;
assert (s_seg = "0001111")
report "Simulation unsuccessful for input: 7" severity error;

s_hex <= "1000";
wait for 100 ns;
assert (s_seg = "0000000")
report "Simulation unsuccessful for input: 8" severity error;

s_hex <= "1001";
wait for 100 ns;
assert (s_seg = "0000100")
report "Simulation unsuccessful for input: 9" severity error;

s_hex <= "1010";
wait for 100 ns;
assert (s_seg = "0001000")
report "Simulation unsuccessful for input: 10" severity error;
```

```

s_hex <= "1011";
wait for 100 ns;
assert (s_seg = "1100000")
report "Simulation unsuccessful for input: 11" severity error;

s_hex <= "1100";
wait for 100 ns;
assert (s_seg = "0110001")
report "Simulation unsuccessful for input: 12" severity error;


s_hex <= "1101";
wait for 100 ns;
assert (s_seg = "1000010")
report "Simulation unsuccessful for input: 13" severity error;

s_hex <= "1110";
wait for 100 ns;
assert (s_seg = "0110000")
report "Simulation unsuccessful for input: 14" severity error;

s_hex <= "1111";
wait for 100 ns;
assert (s_seg = "0111000")
report "Simulation unsuccessful for input: 15" severity error;
wait;
end process p_7seg_decoder;

```
 
## Screenshot with simulated time waveforms



## Listing of VHDL code from source file top.vhd with 7-segment module instantiation

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity top is
    Port (
        SW : in  STD_LOGIC_VECTOR (3 downto 0);

```

```

    LED : out STD_LOGIC_VECTOR (7 downto 0);
    CA  : out STD_LOGIC;
    CB  : out STD_LOGIC;
    CC  : out STD_LOGIC;
    CD  : out STD_LOGIC;
    CE  : out STD_LOGIC;
    CF  : out STD_LOGIC;
    CG  : out STD_LOGIC;
    AN  : out STD_LOGIC_VECTOR (7 downto 0));
end top;

architecture Behavioral of top is

begin
    -- Instance (copy) of hex_7seg entity
    hex2seg : entity work.hex_7seg
        port map(
            hex_i    => SW,
            seg_o(6) => CA,

            seg_o(5) => CB,
            seg_o(4) => CC,
            seg_o(3) => CD,
            seg_o(2) => CE,
            seg_o(1) => CF,
            seg_o(0) => CG
        );

    -- Connect one common anode to 3.3V
    AN <= b"1111_0111";

    -- Display input value
    LED(3 downto 0) <= SW;

    -- Turn LED(4) on if input value is equal to 0, ie "0000"
    LED (4)  <= '1' when (SW = "0000") else '0';

    -- Turn LED(5) on if input value is greater than 9
    LED (5)  <= '1' when (unsigned(SW) > 9) else '0';

    -- Turn LED(6) on if input value is odd, ie 1, 3, 5, ...
    LED (6)  <= '1' when (unsigned(SW) mod 2 = 1) else '0';

    -- Turn LED(7) on if input value is a power of two, ie 1, 2, 4, or 8
    LED (7)  <= '1' when (SW = "0001" or SW = "0010" or SW = "0100" or SW = "1000")
else '0';

end Behavioral;

```

## Truth table for LEDs(7:4)

Hex	Inputs	LED4	LED5	LED6	LED7
0	0000	1	0	0	0
1	0001	0	0	1	1
2	0010	0	0	0	1
3	0011	0	0	1	0
4	0100	0	0	0	1
5	0101	0	0	1	0
6	0110	0	0	0	0
7	0111	0	0	1	0
8	1000	0	0	0	1
9	1001	0	0	1	0
A	1010	0	1	0	0
b	1011	0	1	1	0
C	1100	0	1	0	0
d	1101	0	1	1	0
E	1110	0	1	0	0
F	1111	0	1	1	0

## Listing of VHDL code for LEDs(7:4) with syntax highlighting

```
-- Turn LED(4) on if input value is equal to 0, ie "0000"
LED (4) <= '1' when (SW = "0000") else '0';

-- Turn LED(5) on if input value is greater than 9
LED (5) <= '1' when (unsigned(SW) > 9) else '0';

-- Turn LED(6) on if input value is odd, ie 1, 3, 5, ...
LED (6) <= '1' when (unsigned(SW) mod 2 = 1) else '0';

-- Turn LED(7) on if input value is a power of two, ie 1, 2, 4, or 8
```

```
LED (7) <= '1' when (SW = "0001" or SW = "0010" or SW = "0100" or SW = "1000")
else '0';
```

Screenshot with simulated time waveforms

