

Lab assignment 07 - Flip-Flops

Prep. task -

Characteristic equations

```

-----
--D flip-flop:
 $q_{(n+1)} = d$ 
-----
--JK flip-flop:
 $q_{(n+1)} = j * (\text{not } q_n) + (\text{not } k) * q_n$ 
-----
--T flip-flop:
 $q_{(n+1)} = t * (\text{not } q_n) + (\text{not } t) * q_n$ 

```

Completed tables for D, JK, T flip-flops

D	Qn	Q(n+1)	Comments
0	0	0	No change
0	1	0	Change
1	1	1	No change
1	0	1	Change

J	K	Qn	Q(n+1)	Comments
0	0	0	0	No change
0	0	1	1	No change
0	1	0	0	Reset
0	1	1	0	Reset
1	0	0	1	Set
1	0	1	1	Set
1	1	0	1	Toggle

J	K	Qn	Q(n+1)	Comments
1	1	1	0	Toggle

T	Qn	Q(n+1)	Comments
0	0	0	No change
0	1	1	No change
1	0	1	Toggle
1	1	0	Toggle

D latch

VHDL code listing of the process `p_d_latch` with syntax highlighting

```
p_d_latch : process (en, d, arst)
begin
    if(arst = '1') then
        q      <= '0';
        q_bar <= '1';
    elsif (en = '1') then
        q      <= d;
        q_bar <= not d;
    end if;
end process p_d_latch;
```

Listing of VHDL reset and stimulus processes from the testbench `tb_d_latch.vhd` file with syntax highlighting and asserts

```
p_stimulus : process
begin

    s_en      <= '0';
    s_d       <= '0';
    s_arst    <= '0';
    wait for 10 ns;

    s_d       <= '1';
    wait for 20 ns;
    s_d       <= '0';
    wait for 20 ns;
```

```

s_d      <= '1';
wait for 20 ns;
s_d      <= '0';
wait for 20 ns;
assert (s_q = '1' and s_q_bar = '0') report "EMPTY SEQUENCE ERROR" severity
error;
--sequence with enable active
-----
s_en     <= '1';      --enabled
-----
s_d      <= '1';
wait for 20 ns;
-----
s_en     <= '1';      --enabled
-----
s_d      <= '0';
wait for 20 ns;
-----
s_en     <= '1';      --enabled
-----
s_d      <= '1';
wait for 20 ns;
-----
s_en     <= '1';      --enabled
-----
s_d      <= '0';
wait for 20 ns;
assert (s_q = '1' and s_q_bar = '0') report "ENABLE SEQUENCE ERROR" severity
error;
--sequence with enable and reset active
-----
s_en     <= '1';      --enabled
-----
s_arst   <= '1';      --reset
s_d      <= '1';
wait for 20 ns;
-----
s_en     <= '1';      --enabled
-----
s_arst   <= '1';      --reset
s_d      <= '0';
wait for 20 ns;
-----
s_en     <= '1';      --enabled
-----
s_arst   <= '1';      --reset
s_d      <= '1';
wait for 20 ns;
-----
s_en     <= '1';      --enabled
-----


```

```

s_arst <= '1';    --reset
s_d    <= '0';
wait for 20 ns;
-----
s_en   <= '0';    --enabled
-----
s_arst <= '1';    --reset
s_d    <= '1';
wait for 20 ns;
-----
s_en   <= '1';    --enabled
-----
s_arst <= '0';    --reset
s_d    <= '1';
wait for 20 ns;
assert (s_q = '1' and s_q_bar = '0') report "ENABLE AND RESET SEQUENCE ERROR"
severity error;
wait;

```

 Screenshot with simulated time waveforms - for D latch



Flip-flops

VHDL code listing of the processes with syntax highlighting

p_d_ff_arst - design process

```

p_d_ff_arst : process(clk, arst)
begin
    if (arst = '1') then
        q      <= '0';
        q_bar  <= '1';
    elsif rising_edge(clk) then
        q      <= d;
        q_bar  <= not d;
    end if;
end process p_d_ff_arst;

```

tb_d_ff_arst - process from testbench

```

p_d_ff_arst :process
begin
    s_d    <= '1';
    wait for 20 ns;
    assert (s_q = '1' and s_q_bar = '0') report "ERROR - FIRST FLIP" severity
note;

    s_d    <= '0';
    wait for 20 ns;
    assert (s_q = '0' and s_q_bar = '1') report "ERROR - FIRST FLIP" severity
note;

    s_d    <= '1';
    wait for 20 ns;
    assert (s_q = '1' and s_q_bar = '0') report "ERROR - 2. FLIP" severity
note;

    s_d    <= '0';
    wait for 20 ns;
    assert (s_q = '0' and s_q_bar = '1') report "ERROR - 2. FLIP" severity
note;

    s_d    <= '1';
    wait for 20 ns;
    assert (s_q = '1' and s_q_bar = '0') report "ERROR - 3. FLIP" severity
note;

    s_d    <= '0';
    wait for 20 ns;
    assert (s_q = '0' and s_q_bar = '1') report "ERROR - 3. FLIP" severity
note;


    s_d    <= '1';
    wait for 20 ns;
    assert (s_q = '1' and s_q_bar = '0') report "ERROR - 4. FLIP" severity
note;

    s_d    <= '0';
    wait for 20 ns;
    assert (s_q = '0' and s_q_bar = '1') report "ERROR - 4. FLIP" severity
note;

    wait;
end process p_d_ff_arst;

```

 Screenshot with simulated time waveforms - for D flip-flop (async reset)



p_d_ff_rst - design process

```
p_d_ff_rst : process(clk)
begin
    if rising_edge(clk) then
        if (rst = '1') then
            q      <= '0';
            q_bar  <= '1';
        else
            q      <= d;
            q_bar  <= not d;
        end if;
    end if;
end process p_d_ff_rst;
```

tb_d_ff_rst - process from testbench

```
p_d_ff_rst : process
begin

    s_d      <= '1';
    wait for 20 ns;
    assert (s_q = '1' and s_q_bar = '0') report "ERROR - FIRST FLIP" severity
note;

    s_d      <= '0';
    wait for 20 ns;
    assert (s_q = '0' and s_q_bar = '1') report "ERROR - FIRST FLIP" severity
note;

    s_d      <= '1';
    wait for 20 ns;
    assert (s_q = '1' and s_q_bar = '0') report "ERROR - 2. FLIP" severity
note;

    s_d      <= '0';
    wait for 20 ns;
    assert (s_q = '0' and s_q_bar = '1') report "ERROR - 2. FLIP" severity
note;

    s_d      <= '1';
    wait for 20 ns;
    assert (s_q = '1' and s_q_bar = '0') report "ERROR - 3. FLIP" severity
note;

    s_d      <= '0';
    wait for 20 ns;
    assert (s_q = '0' and s_q_bar = '1') report "ERROR - 3. FLIP" severity
```

```

note;

s_d    <= '1';
wait for 20 ns;
assert (s_q = '1' and s_q_bar = '0') report "ERROR - 4. FLIP" severity
note;


s_d    <= '0';
wait for 20 ns;
assert (s_q = '0' and s_q_bar = '1') report "ERROR - 4. FLIP" severity
note;

wait;

end process p_d_ff_rst;

```

 Screenshot with simulated time waveforms - for D flip-flop (sync reset)



p_jk_ff_rst - design process

```

p_jk_ff_rst : process(clk)
begin
    if rising_edge(clk) then
        if (rst = '1') then
            s_q    <= '0';
            s_q_bar <= '1';
        else
            if (j = '0' and k = '0') then
                s_q    <= s_q;
                s_q_bar <= s_q_bar;
            elsif (j = '0' and k = '1') then
                s_q    <= '0';
                s_q_bar <= '1';
            elsif (j = '1' and k = '0') then
                s_q    <= '1';
                s_q_bar <= '0';
            end if;
        end if;
    end if;
end process;

```

```

        else
            s_q      <= not s_q;
            s_q_bar <= not s_q_bar;
        end if;
    end if;
end if;
end process p_jk_ff_rst;

```

tb_jk_ff_rst - process from testbench

```

p_jk_ff_rst :process
begin

    s_j <= '1';
    s_k <= '0';
    wait for 10ns;
    assert (s_q = '1' and s_q_bar = '0') report "FIRST SET ERROR" severity
error;

    s_j <= '1';
    s_k <= '1';
    wait for 10ns;
    assert (s_q = '0' and s_q_bar = '1') report "FIRST TOGGLE ERROR" severity
error;

    s_j <= '0';
    s_k <= '1';
    wait for 10ns;
    assert (s_q = '0' and s_q_bar = '1') report "FIRST RESET ERROR" severity
error;

    s_j <= '1';
    s_k <= '1';
    wait for 10ns;
    assert (s_q = '1' and s_q_bar = '0') report "2. TOGGLE ERROR - acceptable"
severity error;    --error reported because reset is active

    s_j <= '0';
    s_k <= '1';
    wait for 10ns;
    assert (s_q = '0' and s_q_bar = '1') report "2. RESET ERROR" severity
error;

    s_j <= '1';
    s_k <= '1';
    wait for 10ns;
    assert (s_q = '1' and s_q_bar = '0') report "3. TOGGLE ERROR" severity

```



```

error;


s_j <= '1';
s_k <= '1';
wait for 10ns;
assert (s_q = '0' and s_q_bar = '1') report "4. TOGGLE ERROR" severity
error;

s_j <= '1';
s_k <= '0';
wait for 10ns;
assert (s_q = '1' and s_q_bar = '0') report "2. SET ERROR" severity error;
wait;

end process p_jk_ff_rst;

```

 Screenshot with simulated time waveforms - for JK flip-flop (sync reset)



p_t_ff_rst - design process

```

p_t_ff_rst : process(clk)
begin
    if rising_edge(clk) then
        if (rst = '1') then
            s_q      <= '0';
            s_q_bar  <= '1';

        else
            if (t = '0') then
                s_q      <= s_q;
                s_q_bar  <= s_q_bar;

            else
                s_q      <= not s_q;
                s_q_bar  <= not s_q_bar;
            end if;
        end if;
    end if;
end process;

```

```

        end if;
    end process p_t_ff_rst;

```

tb_t_ff_rst - process from testbench

```

p_t_ff_arst : process
begin

    s_t <= '1';
    wait for 10ns;
    assert (s_q = '0' and s_q_bar = '1') report "FIRST TOGGLE ERROR" severity
error; -- reset active

    s_t <= '0';
    wait for 10ns;
    assert (s_q = '0' and s_q_bar = '1') report "FIRST NO CHANGE ERROR"
severity error; -- reset was active

    s_t <= '1';
    wait for 10ns;
    assert (s_q = '1' and s_q_bar = '0') report "2. TOGGLE ERROR" severity
error;

    s_t <= '1';
    wait for 10ns;
    assert (s_q = '0' and s_q_bar = '1') report "3. TOGGLE ERROR" severity
error;

    s_t <= '0';
    wait for 10ns;
    assert (s_q = '0' and s_q_bar = '1') report "2. NO CHANGE ERROR" severity
error;

    s_t <= '1';
    wait for 10ns;
    assert (s_q = '1' and s_q_bar = '0') report "4. TOGGLE ERROR" severity
error;

    s_t <= '0';
    wait for 10ns;
    assert (s_q = '1' and s_q_bar = '0') report "3. NO CHANGE ERROR" severity
error;
    wait;

    s_t <= '0';
    wait for 10ns;
    assert (s_q = '1' and s_q_bar = '0') report "4. NO CHANGE ERROR" severity
error;

```


```

s_t <= '1';
wait for 10ns;
assert (s_q = '0' and s_q_bar = '1') report "5. TOGGLE ERROR" severity
error;

end process p_t_ff_arst;

```

 Screenshot with simulated time waveforms - for T flip-flop (sync reset)



Listing of VHDL clock and reset from the testbench files with syntax highlighting

Clock (is same in every file)

```

p_clk_gen : process
begin
    while now < 750 ns loop          -- 75 periods of 100MHz clock
        s_clk <= '0';
        wait for c_CLK_100MHZ_PERIOD / 2;
        s_clk <= '1';
        wait for c_CLK_100MHZ_PERIOD / 2;
    end loop;
    wait;
end process p_clk_gen;

```

Reset (is same in every file, except tb_t_ff_rst.vhd - is shown separately)

```

p_reset_gen : process
begin
    s_arst <= '0';
    wait for 20 ns;
    s_arst <= '1';          -- Reset activated
    wait for 30 ns;
    s_arst <= '0';
    wait;
end process p_reset_gen;

```

Reset for tb_t_ff_rst.vhd

```
p_reset_gen : process
begin
    s_rst <= '0';
    wait for 1 ns;
    s_rst <= '1';           -- Reset activated
    wait for 10 ns;
    s_rst <= '0';
    wait;
end process p_reset_gen;
```

Shift register

Image of the shift register schematic

